

```

timescale 1ns / 1ps
/*****
* Module: debounced
*
* Author: Noah Hanks
* Class: ECEN 220, Section 3, Fall 2020 - ECEN 220, Section 1, Winter 2020 * Date: 3
November 2020
*
* Description: Uses a counter to determine how long a button has been pressed to
tell if the button bounced or not.
*
*
*****/
`default_nettype none
module debounce(
    input wire logic clk, reset, noisy,
    output logic debounced
);

    logic timerDone, clrTimer;
    logic[18:0] extra;
    typedef enum logic[1:0] {s0, s1, s2, s3, ERR='X} StateType;
    StateType ns, cs;

    mod_counter #(500000, 19) MC0(.clk(clk), .reset(clrTimer), .increment(1'b1),
    .rolling_over(timerDone), .count(extra));

    //this block determines if the button is help long enough to be counted as a single
input.
    //otherwise, it says that the input was never made because the value of noisy
changed too fast.
    always_comb begin
        ns = ERR;
        debounced = 0;
        clrTimer = 0;
        if(reset)
            ns = s0;
        else
            case(cs)
            s0: begin
                clrTimer = 1'b1;
                if(noisy)
                    ns = s1;
                else
                    ns = s0;
            end

```

```

s1: if(noisy & timerDone)
    ns = s2;
else if(noisy & ~timerDone)
    ns = s1;
else
    ns = s0;
s2: begin
    debounced = 1'b1;
    clrTimer = 1'b1;
    if(noisy)
        ns = s2;
    else
        ns = s3;
    end
s3: begin
    ns = s3;
    debounced = 1'b1;
    if(~noisy & ~timerDone)
        ns = s3;
    else if(noisy)
        ns = s2;
    else
        ns = s0;
    end
endcase
end

```

```

//this block makes sure the current state is always being set to the next state
always_ff @(posedge clk)
cs <= ns;

```

```

endmodule

```